

# Mathematics for Computer Science final exam

소프트웨어학부 컴퓨터과학과  
2016133 이유진

# Software Design

Graph Algorithm


Step #1: Find two cases of shortest time path from a starting point to an arrival point

Comparison between two paths					
Case	Starting point	Arrival point	Item	Shortest time path found via naver-search	Shortest time path found via your method using Dijkstra's algorithm
Case #1	중곡	왕십리	Path	왕십리 - 마장 - 답십리 - 장한평 - 군자 - 중곡	
			Time		
Case #2	화곡	온수	Path	화곡 - 까치산 - 신정 - 목동 - 오목 교 - 양평 - 영등포구청 - 영등포시 장 - 신길 - 영등포 - 구로 - 구일 - 개봉 - 오류동 - 온수	
			Time		

Step #1-1: If you find any difference between two paths, explain why the difference arises.


# Step #2: Build two cases of simple & weighted graph model

Case #1

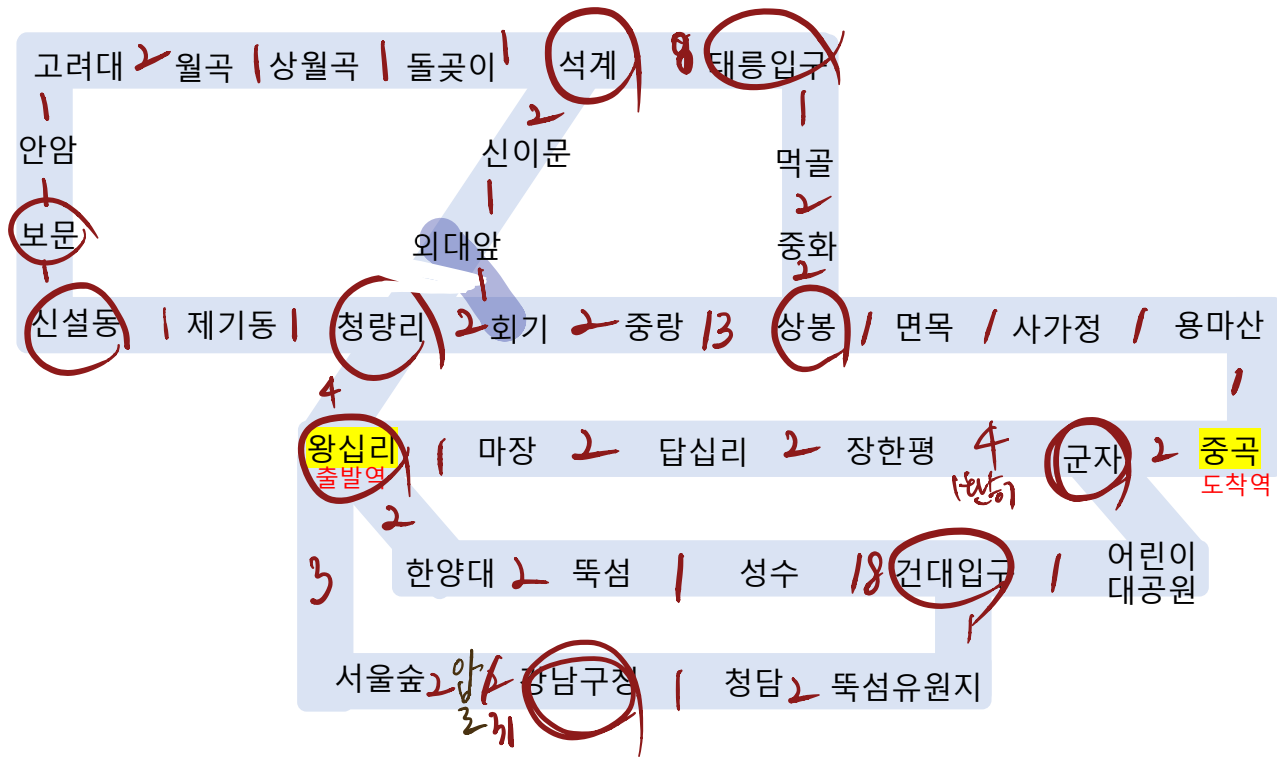

# Step #2: Build two cases of simple & weighted graph model

Case #2

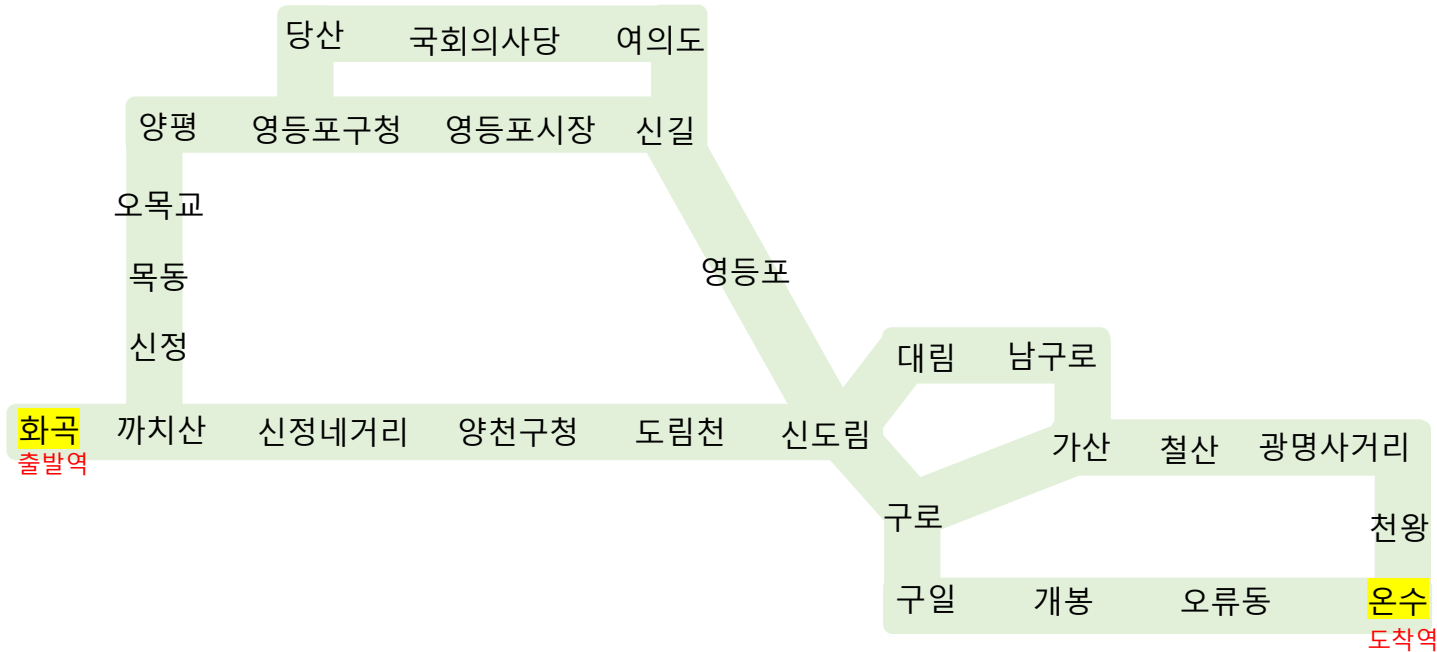

Step #3: Show the entire process of Dijkstra's algorithm for each case

Step #4: Let's consider subway accidents as below



Step #4-1: Let's assume subway accident stopping operation of a station

Step #4-2-1: Find 3 cases of shortest path in Case #1


Step #4-2-2: Find 3 cases of shortest path in Case #2

# Step #4-3: Tuning Dijkstra's algorithm
 
# Hardware Design

Digital circuit based on boolean algebra

Step #1: Propose a way to represent hexadecimal number on 12-segment display



New display built on decimal number display

111111000000	011000000000	110110110000	111100110000	011001110000
101101110000	101111110000	111000000000	111111110000	111101110000
000011101010	100111100110	100111000000	000011001001	100111110000

Step #2: Fill the below blank with your definition based on your proposal

Hexadecimal Number	Input (4-bit)				Output (Your definition)											
	w	x	y	z	a	b	c	d	e	f	g	h	i	j	k	l
0	0	0	0	0	1	1	1	1	1	1	0	0	0	0	0	0
1	0	0	0	1	0	1	1	0	0	0	0	0	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1	1	0	0	0	0
3	0	0	1	1	1	1	1	1	0	0	1	1	0	0	0	0
4	0	1	0	0	0	1	1	0	0	1	1	1	0	0	0	0
5	0	1	0	1	1	0	1	1	0	1	1	1	0	0	0	0
6	0	1	1	0	1	0	1	1	1	1	1	1	0	0	0	0
7	0	1	1	1	1	1	1	0	0	0	0	0	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1	1	0	0	0	0
9	1	0	0	1	1	1	1	1	0	1	1	1	0	0	0	0
A	1	0	1	0	0	0	0	0	1	1	1	0	1	0	1	0
B	1	0	1	1	1	0	0	1	1	1	1	0	0	1	1	0
C	1	1	0	0	1	0	0	1	1	1	0	0	0	0	0	0
D	1	1	0	1	0	0	0	0	1	1	0	0	1	0	0	1
E	1	1	1	0	1	0	0	1	1	1	1	1	0	0	0	0
F	1	1	1	1	1	0	0	0	1	1	1	1	0	0	0	0

Step #3: Design BCHD(Binary Coded HexaDemical) to 12 Segment display decoder.

Output 'a'

Combinational logic design process

Step #1

Hexadecimal Number	Input (4-bit)				Output
	w	x	y	z	
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
A	1	0	1	0	0
B	1	0	1	1	1
C	1	1	0	0	1
D	1	1	0	1	0
E	1	1	1	0	1
F	1	1	1	1	1

Step #2

yz \ wx	00	01	11	10
00	1		1	1
01		1	1	1
11	1		1	1
10	1	1	1	

$$\begin{aligned} a &= w'x'y'z' + w'x'yz' + w'x'yz' \\ &\quad + w'xy'z' + wxyz' + wxyz' \\ &\quad + wx'y'z' + wx'y'z + wx'y'z \\ &= (wy'z' + x'y'z') + w'y + w'xz + xy \\ &\quad + (wx'y' + wxz) \end{aligned}$$

Step #3



# Step #3: Design BCHD(Binary Coded HexaDemical) to 12 Segment display decoder.

## Output 'b'

### Combinational logic design process

#### Step #1


Hexadecimal Number	Input (4-bit)				Output
	w	x	y	z	
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
A	1	0	1	0	0
B	1	0	1	1	0
C	1	1	0	0	0
D	1	1	0	1	0
E	1	1	1	0	0
F	1	1	1	1	0

#### Step #2

yz \ wx	00	01	11	10
00	1	1	1	1
01	1		1	
11				
10	1	1		

$$\begin{aligned}
 b &= w'x'y'z' + w'x'y'z + w'x'yz + w'xy'z' \\
 &\quad + w'xy'z + wxyz \\
 &\quad + wx'y'z' + wx'y'z \\
 &= w'x' + x'y' + w'y'z' + w'yz
 \end{aligned}$$

#### Step #3

 

Step #3: Design BCHD(Binary Coded HexaDemical) to 12 Segment display decoder.

Output 'c'

Combinational logic design process

Step #1

Hexadecimal Number	Input (4-bit)				Output
	w	x	y	z	
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	0
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
A	1	0	1	0	0
B	1	0	1	1	0
C	1	1	0	0	0
D	1	1	0	1	0
E	1	1	1	0	0
F	1	1	1	1	0

Step #2

yz \ wx	00	01	11	10
00	1	1	1	
01	1	1	1	1
11				
10		1	1	

$$\begin{aligned} c &= w'x'y'z' + w'x'y'z + w'x'yz \\ &\quad + w'xy'z' + w'xy'z + w'xyz + w'xyz' \\ &\quad + wx'y'z' + wx'y'z \\ &= x'y' + w'y' + w'z + w'x \end{aligned}$$

Step #3

Step #3: Design BCHD(Binary Coded HexaDemical) to 12 Segment display decoder.

Output 'd'

Combinational logic design process

Step #1

Hexadecimal Number	Input (4-bit)				Output
	w	x	y	z	
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	1
A	1	0	1	0	0
B	1	0	1	1	1
C	1	1	0	0	1
D	1	1	0	1	0
E	1	1	1	0	1
F	1	1	1	1	0

Step #2

yz \ wx	00	01	11	10
00	1		1	1
01		1		1
11	1			1
10	1	1	1	

$$\begin{aligned} d &= w'x'y'z' + w'x'yz' + w'xy'z' \\ &\quad + w'xy'z + w'xyz' \\ &\quad + wx'y'z' + wxyz' \\ &\quad + wx'y'z + wx'y'z + wx'yz + wx'yz' \\ &= w'x'y + (wy'z' + x'y'z') + w'xy'z \\ &\quad + xyz' + wx'z \end{aligned}$$

Step #3

# Step #3: Design BCHD(Binary Coded HexaDemical) to 12 Segment display decoder.

## Output 'e'

### Combinational logic design process

#### Step #1


Hexadecimal Number	Input (4-bit)				Output
	w	x	y	z	
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	0
A	1	0	1	0	1
B	1	0	1	1	1
C	1	1	0	0	1
D	1	1	0	1	1
E	1	1	1	0	1
F	1	1	1	1	1

#### Step #2

yz \ wx	00	01	11	10
00	1			1
01				1
11	1	1	1	1
10	1		1	1

$$\begin{aligned}
 e &= w'x'y'z' + w'x'yz' \\
 &\quad + w'xyz' \\
 &\quad + wxy'z' + wxy'z + wxyz + wxyz' \\
 &\quad + wx'y'z' + wx'yz + wx'yz' \\
 &= w'x'z' + yz' + wz' + wx + wy
 \end{aligned}$$

#### Step #3

 

# Step #3: Design BCHD(Binary Coded HexaDemical) to 12 Segment display decoder.

## Output 'f'

### Combinational logic design process

#### Step #1


Hexadecimal Number	Input (4-bit)				Output
	w	x	y	z	
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	1
A	1	0	1	0	1
B	1	0	1	1	1
C	1	1	0	0	1
D	1	1	0	1	1
E	1	1	1	0	1
F	1	1	1	1	1

#### Step #2

yz \ wx	00	01	11	10
00	1			
01	1	1		1
11	1	1	1	1
10	1	1	1	1

$$\begin{aligned}
 f &= w'x'y'z' \\
 &+ w'xy'z' + w'xy'z + w'xyz' \\
 &+ wxy'z' + wxy'z + wxyz + wxyz' \\
 &+ wx'y'z' + wx'y'z + wx'yz + wx'yz' \\
 &= y'z' + (w'x'z' + w'x'y') + w
 \end{aligned}$$

#### Step #3

 

# Step #3: Design BCHD(Binary Coded HexaDemical) to 12 Segment display decoder.

## Output 'g'

### Combinational logic design process

#### Step #1


Hexadecimal Number	Input (4-bit)				Output
	w	x	y	z	
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	1
A	1	0	1	0	1
B	1	0	1	1	1
C	1	1	0	0	0
D	1	1	0	1	0
E	1	1	1	0	1
F	1	1	1	1	1

#### Step #2

wx \ yz	00	01	11	10
00			1	1
01	1	1		1
11			1	1
10	1	1	1	1

$$\begin{aligned}
 g &= w'x'yz + w'x'yz' \\
 &\quad + w'xy'z' + w'xy'z + w'xyz' \\
 &\quad + wxyz + wxz' \\
 &= w'x'y + (w'xy' + w'xz') + wx' + wy
 \end{aligned}$$

#### Step #3

 

Step #3: Design BCHD(Binary Coded HexaDemical) to 12 Segment display decoder.

Output 'h'

Combinational logic design process

Step #1

Hexadecimal Number	Input (4-bit)				Output
	w	x	y	z	
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	1
A	1	0	1	0	0
B	1	0	1	1	0
C	1	1	0	0	0
D	1	1	0	1	0
E	1	1	1	0	1
F	1	1	1	1	1

Step #2

yz \ wx	00	01	11	10
00			1	1
01	1	1		1
11			1	1
10	1	1		

$$\begin{aligned} h &= w'x'yz + w'x'yz' \\ &\quad + w'xy'z' + w'xy'z + w'xyz' \\ &\quad + wxyz + wxyz' \\ &\quad + wx'y'z' + wx'y'z \\ &= w'x'y + (w'xz' + w'xy') + wxy + wx'y' \end{aligned}$$

Step #3

Step #3: Design BCHD(Binary Coded HexaDemical) to 12 Segment display decoder.

Output 'i'

Combinational logic design process

Step #1

Hexadecimal Number	Input (4-bit)				Output
	w	x	y	z	i
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
A	1	0	1	0	1
B	1	0	1	1	0
C	1	1	0	0	0
D	1	1	0	1	1
E	1	1	1	0	0
F	1	1	1	1	0

Step #2

yz \ wx	00	01	11	10
00				
01				
11		1		
10				1

$$i = wxy'z + wx'yz'$$

Step #3

```
graph LR; w((w)) --- AND1[AND]; x((x)) --- AND1; y((y)) --- AND1; z((z)) --- AND1; w --- AND2[AND]; x --- AND2; y --- AND2; z --- AND2; AND1 --- OR[OR]; AND2 --- OR; OR --- i((i));
```



# Step #3: Design BCHD(Binary Coded HexaDemical) to 12 Segment display decoder.

Output 'j'

Combinational logic design process

Step #1

Hexadecimal Number	Input (4-bit)				Output
	w	x	y	z	j
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
A	1	0	1	0	0
B	1	0	1	1	1
C	1	1	0	0	0
D	1	1	0	1	0
E	1	1	1	0	0
F	1	1	1	1	0

Step #2

yz \ wx	00	01	11	10
00				
01				
11				
10			1	

$j = wx'yz$

Step #3

w

x

y

z

j

Step #3: Design BCHD(Binary Coded HexaDemical) to 12 Segment display decoder.

Output 'k'

Combinational logic design process

Step #1

Hexadecimal Number	Input (4-bit)				Output
	w	x	y	z	
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
A	1	0	1	0	1
B	1	0	1	1	1
C	1	1	0	0	0
D	1	1	0	1	0
E	1	1	1	0	0
F	1	1	1	1	0

Step #2

yz \ wx	00	01	11	10
00				
01				
11				
10			1	1

$$k = wx'yz + wx'yz'$$
$$= wx'y$$

Step #3

w

x

y

k

# Step #3: Design BCHD(Binary Coded HexaDemical) to 12 Segment display decoder.

Output 'I'

Combinational logic design process

Step #1

Hexadecimal Number	Input (4-bit)				Output
	w	x	y	z	I
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
A	1	0	1	0	0
B	1	0	1	1	0
C	1	1	0	0	0
D	1	1	0	1	1
E	1	1	1	0	0
F	1	1	1	1	0

Step #2

yz \ wx	00	01	11	10
00				
01				
11		1		
10				

I = wx y' z

Step #3

```
graph LR; w --- AND; x --- AND; y --- NOT --- AND; z --- AND; AND --- I
```

Step #4: Explain meaning of the designed BCD to 12 segment display order